

1993 Paper 1 Question 3

Explain the *Synchronization Problem* which affects the operation of certain logic circuits. How should circuits be designed to minimize or avoid the problem?