

1994 Paper 1 Question 1

An UP-DOWN binary counter with input A is required. If $A=0$ the counter counts up, and if $A=1$ it counts down. Design an implementation for 3 bits using T-type flipflops. [20 marks]