

2000 Paper 9 Question 2

VLSI Design

Sketch a transistor-level design and give a brief description of the method of operation for each of the following memory cells:

(a) a dual-ported, static memory cell [5 marks]

(b) a dynamic memory cell using standard MOS logic [5 marks]

(c) a dynamic memory cell for dense memory [5 marks]

Explain the comparative merits of the three designs and explain where they might be used. [5 marks]