

## 2007 Paper 7 Question 11

### VLSI Design

- (a) Sketch a transistor-level circuit for a 2-input AND gate in static CMOS. [2 marks]
- (b) Consider the design of a 16-input AND gate in static CMOS.
- (i) Explain why the 2-input design could not simply be scaled up. [2 marks]
  - (ii) Sketch alternative designs using two and four levels of NAND and NOR gates. [2 × 2 marks]
  - (iii) Use logical effort to estimate the delay of both the designs, assuming that the conducting channel in a pFET has twice the resistance of that in an nFET. [10 marks]
  - (iv) Determine the approximate value of the electrical effort at which their speeds are equal. [2 marks]