 


11 System-on-Chip Design (DJG)

- (a) Give a basic formula for modelling delay in logic circuits once wiring length is known. [2 marks]
- (b) Give a basic formula for modelling power consumption in logic circuits once wiring length is known. [2 marks]
- (c) The figure below gives two versions of a finite-state machine before and after a modification.



Give the name of this modification, say why is it performed and fully explain the role of the additional latch. [4 marks]

- (d) Three power saving techniques used in current SoCs are dynamic voltage and frequency scaling (DVS), clock gating and power supply gating. Compare and contrast these three techniques in terms of
  - (i) physical granularity [3 marks]
  - (ii) temporal granularity [3 marks]
  - (iii) the manual complexity they add to the design flow [3 marks]
- (e) Including power consumption, discuss what design considerations result in a product using an FPGA (field-programmable gate array) rather than an application-specific integrated circuit (ASIC)? [3 marks]

[Note: In all sections, marks will be awarded for sensible argument even if assumptions or results are incorrect.]