

COMPUTER SCIENCE TRIPOS Part IA – 2025 – Paper 2

1 Digital Electronics (ijw24)

(a) Show algebraically that the following functions can be implemented using either a 2-input exclusive OR gate or its complement.

(i)  $F(X, Y) = X.Y \oplus (X + Y)$

(ii)  $G(A, B) = A \oplus B \oplus (A + B) + \overline{A}. \overline{B}$

[4 marks]

(b) (i) Show how the following function may be implemented using an AND gate, an OR gate and an XOR gate, all having two inputs.


$$H(A, B, C, D) = \overline{A}.C + \overline{A}.D + \overline{B}.C + \overline{B}.D + A.B.\overline{C}.\overline{D}$$

[3 marks]

(ii) Show how the function in Part (b)(i) may be implemented using a 16:1 multiplexer. Use variable  $A$  as the most significant bit of the multiplexer control inputs. [2 marks]

(iii) With the aid of a truth-table, show how the function in Part (b)(i) may alternatively be implemented using an 8:1 multiplexer and a NOT gate. Use variables  $A, B$  and  $C$  as the control inputs, where  $A$  is the most significant bit. Assume that complemented input variables are *not* available. [4 marks]

 (c) For the following circuit, assume that all the logic gates have an equal value of *non-zero* propagation delay and that  $P = 1$  and  $Q = 1$



(i) Describe what happens at output  $Y$  when input  $S$  changes from 1 to 0.

(ii) Show how the undesirable change observed at  $Y$  in Part (c)(i) may be removed. [7 marks]